ASVAB-SECTION-5^{Q&As}

ASVAB Section Five: Electronic Information

Pass ASVAB ASVAB-SECTION-5 Exam with 100% Guarantee

Free Download Real Questions & Answers PDF and VCE file from:

https://www.leads4pass.com/asvab-section-5.html

100% Passing Guarantee 100% Money Back Assurance

Following Questions and Answers are all new published by ASVAB
Official Exam Center

- Instant Download After Purchase
- 100% Money Back Guarantee
- 365 Days Free Update
- 800,000+ Satisfied Customers





https://www.leads4pass.com/asvab-section-5.html 2024 Latest leads4pass ASVAB-SECTION-5 PDF and VCE dumps Download

QUESTION 1

| An AA battery produces a potential difference of 1.5 V. Four AA batteries are placed in series to power a portable FM radio. |
|--|
| What is the total voltage of the radio? |
| A. 0.75 V |
| B. 1.5 V |
| C. 3.0 V |
| D. 6.0 V |
| Correct Answer: D |
| Voltages in series are added to determine the total voltage. 1.5 V + 1.5 V + 1.5 V + 1.5 V = 6.0 V. |
| |
| QUESTION 2 |
| 16-gauge wire is than 12-gauge wire. |
| A. less flexible |
| B. more flexible |
| C. thinner |
| D. thicker |
| Correct Answer: C |
| 16-gauge wire is thinner than 12-gauge wire ?the larger the gauge number, the thinner the wire. |
| |
| QUESTION 3 |
| How many paths of electrical flow can be found in a series circuit? |
| A. one |
| B. two |
| C. two or more |
| D. It can\\'t be determined from the information given. |
| Correct Answer: A |

An example of a series circuit would be a string of Christmas lights. If you break the circuit\\'s path at any point,

electricity will stop flowing and the lights will not work.

https://www.leads4pass.com/asvab-section-5.html

2024 Latest leads4pass ASVAB-SECTION-5 PDF and VCE dumps Download

QUESTION 4

How much voltage has a typical home outlet?

- A. 120 volts
- B. 200 volts
- C. 60 volts
- D. 100 volts

Correct Answer: A

A typical residential electrical outlet has 120 volts.

QUESTION 5



The symbol above represents a _____.



https://www.leads4pass.com/asvab-section-5.html 2024 Latest leads4pass ASVAB-SECTION-5 PDF and VCE dumps Download

A. thyristor

B. resistor

C. transistor

D. fuse

Correct Answer: B

The symbol shown represents a resistor.

Latest ASVAB-SECTION-5 <u>Dumps</u>

ASVAB-SECTION-5 VCE <u>Dumps</u>

ASVAB-SECTION-5 Practice Test